



ELEKTRONIKA ANALOG

Pertemuan 5 – Transistor



Frida Hasana, S.Pd., M.Eng.



Transistor: Tipe

1

BJT

BIPOLAR JUNCTION TRANSISTOR



2

FET



FIELD EFFECT TRANSISTOR

Transistor: BJT

NPN

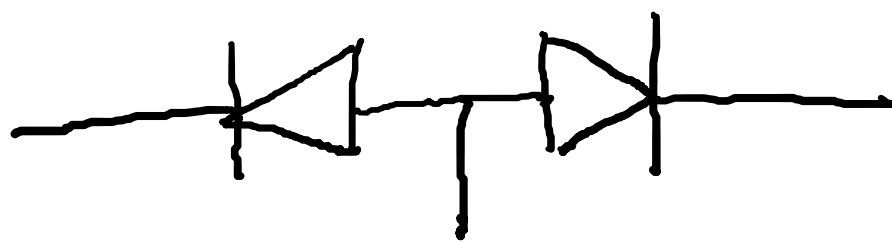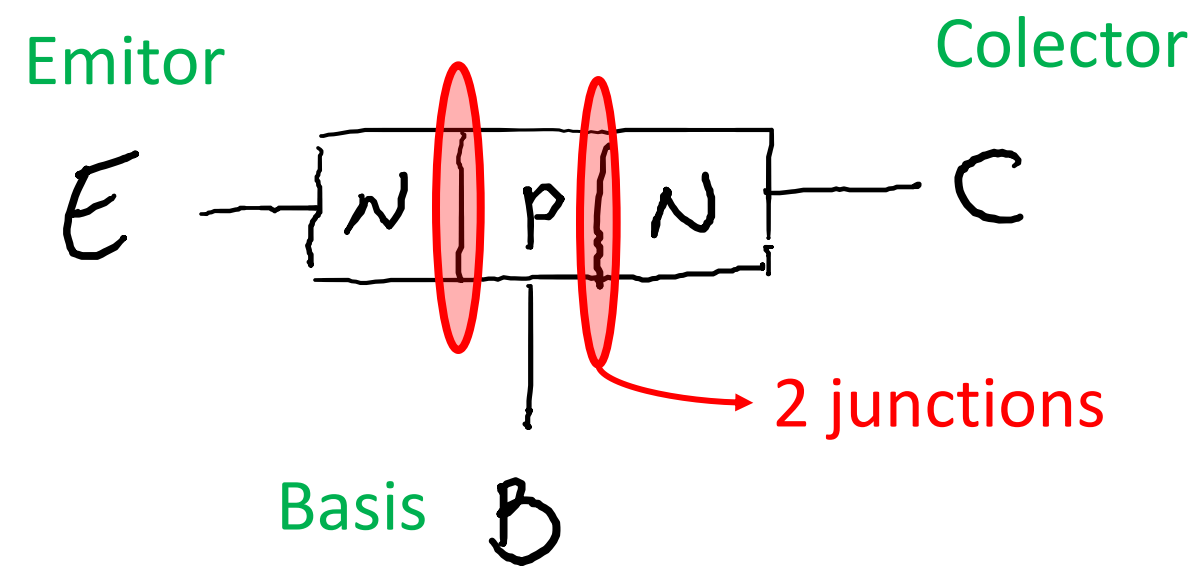


PNP

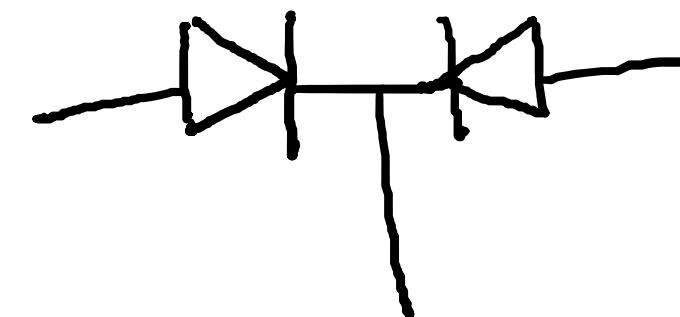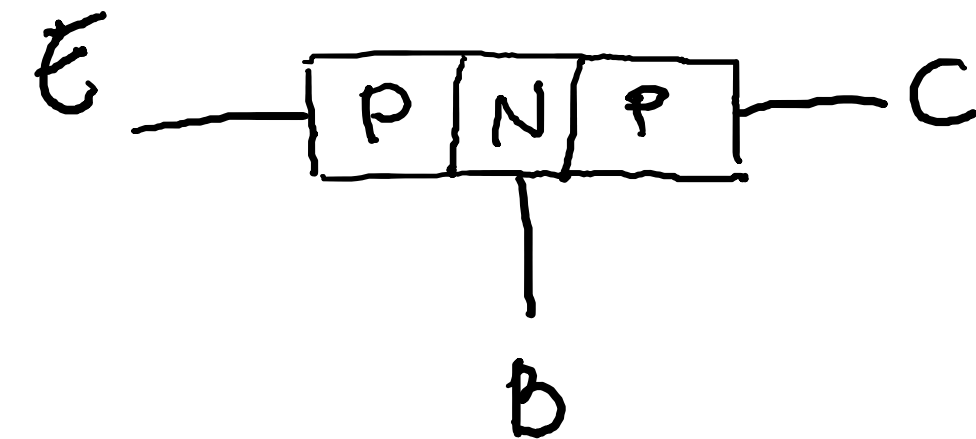


Transistor: Symbol

NPN

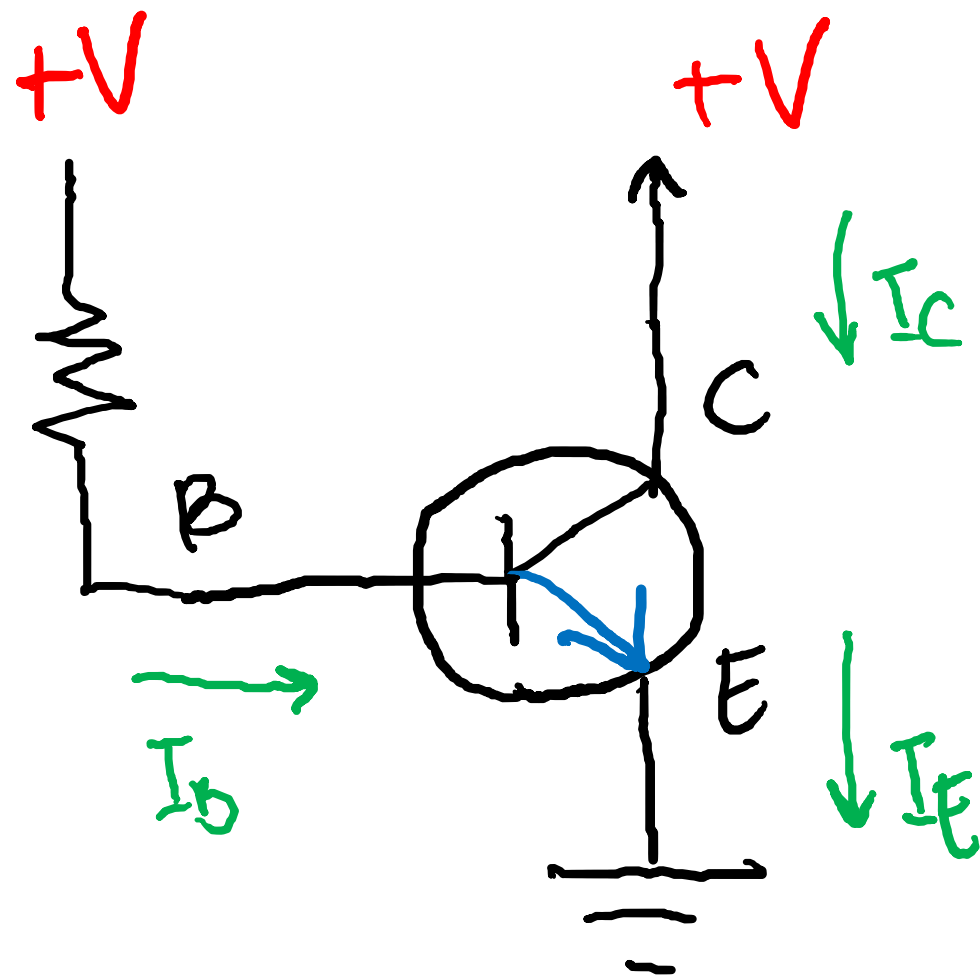

PNP

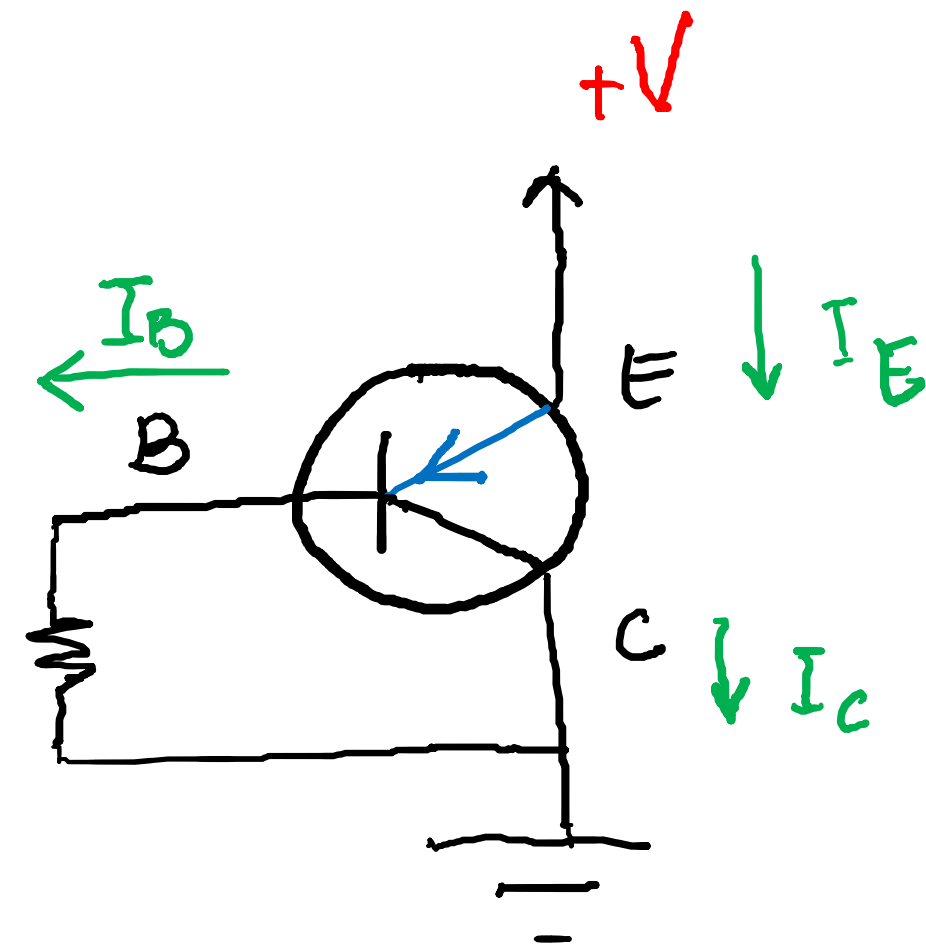


COMPLETELY
OPPOSITE

- Arus mengalir dari positif ke negatif
- Arrow = Emitter

Transistor: NPN

NPN

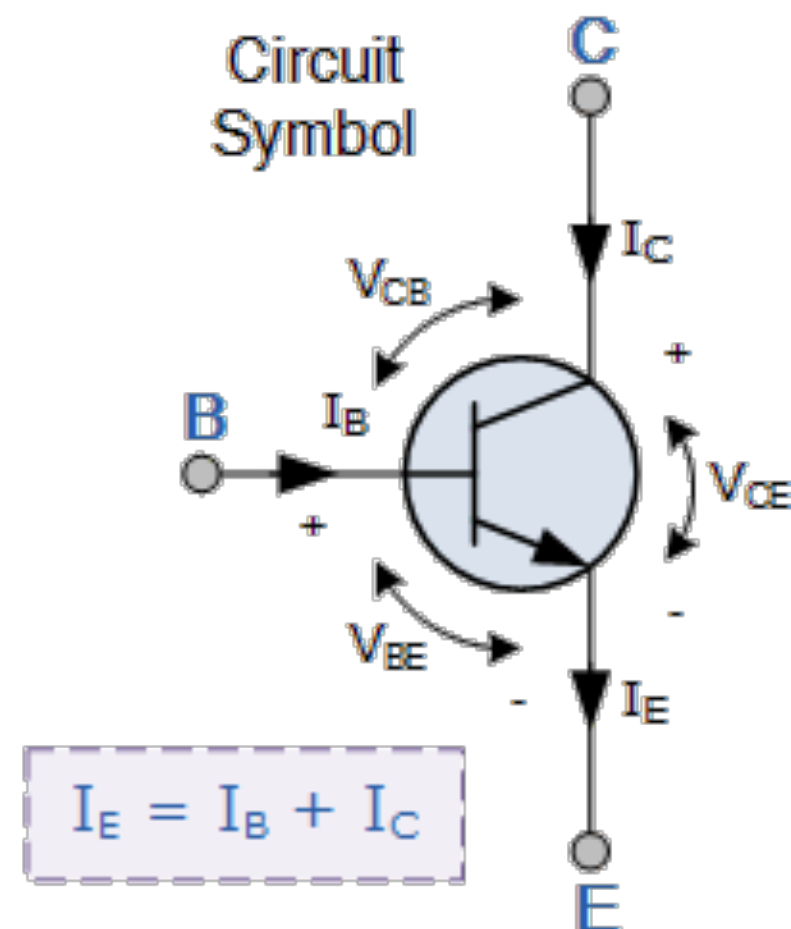

$$I_C = \beta \cdot I_B$$

$$\beta = h_{fe}$$

$$I_E = I_C + I_B$$


$$I_E = \beta \cdot I_B + I_B$$

$$I_E = I_B (\beta + 1)$$

Transistor: NPN

$$1000 \mu A = 1 \text{ mA}$$

$$I_E \approx I_C$$

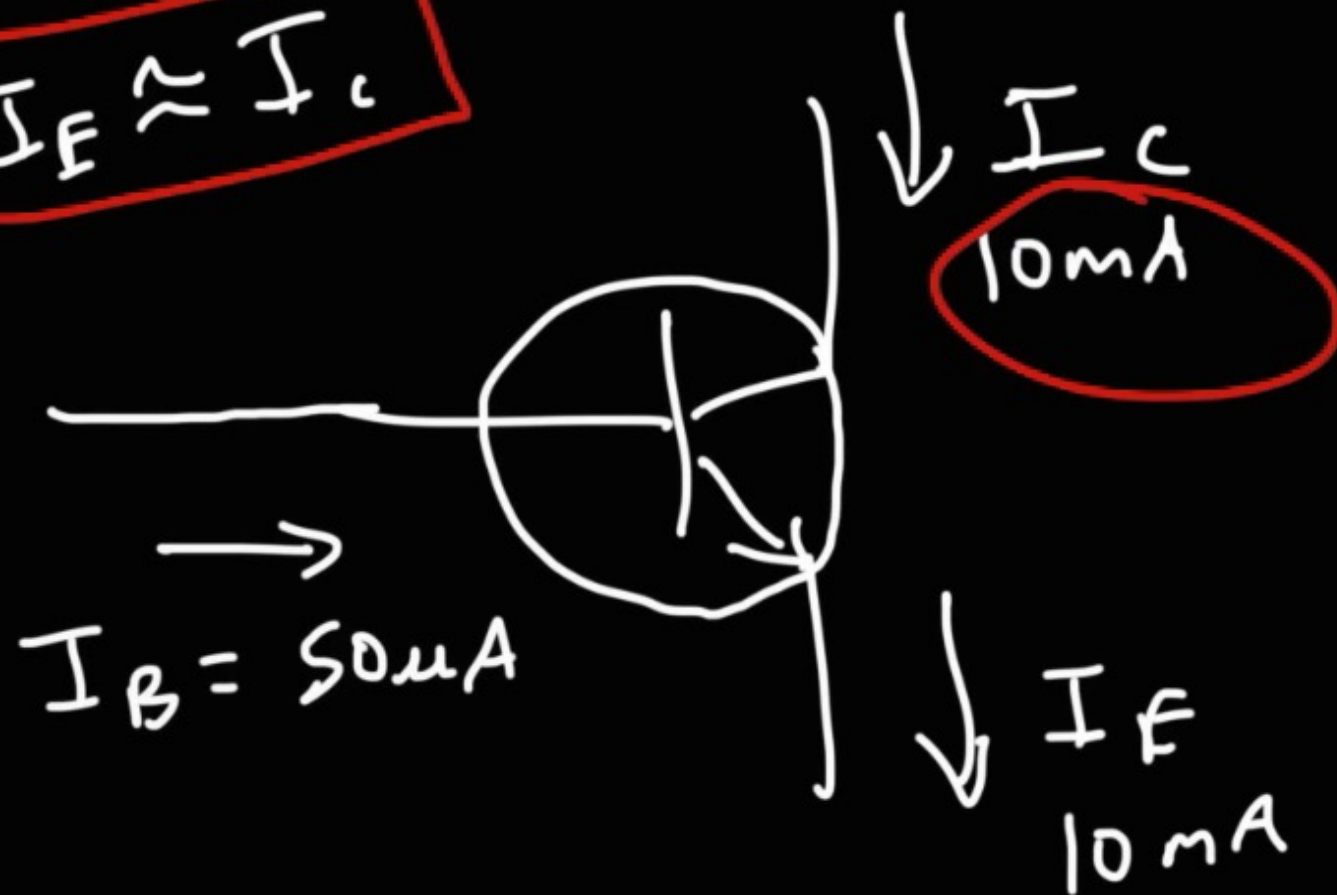

$$h_{fe} = 200$$
$$h_{fe} > 1000$$

$$I_C = \beta I_B$$

$$I_C = 200(50 \mu A)$$


$$I_C = 10,000 \mu A$$

$$I_C = 10 \text{ mA}$$

$$I_E = I_B + I_C$$

$$= 50 \mu A + 10,000 \mu A = 10,050 \mu A = 10.05 \text{ mA}$$

Transistor: Identification

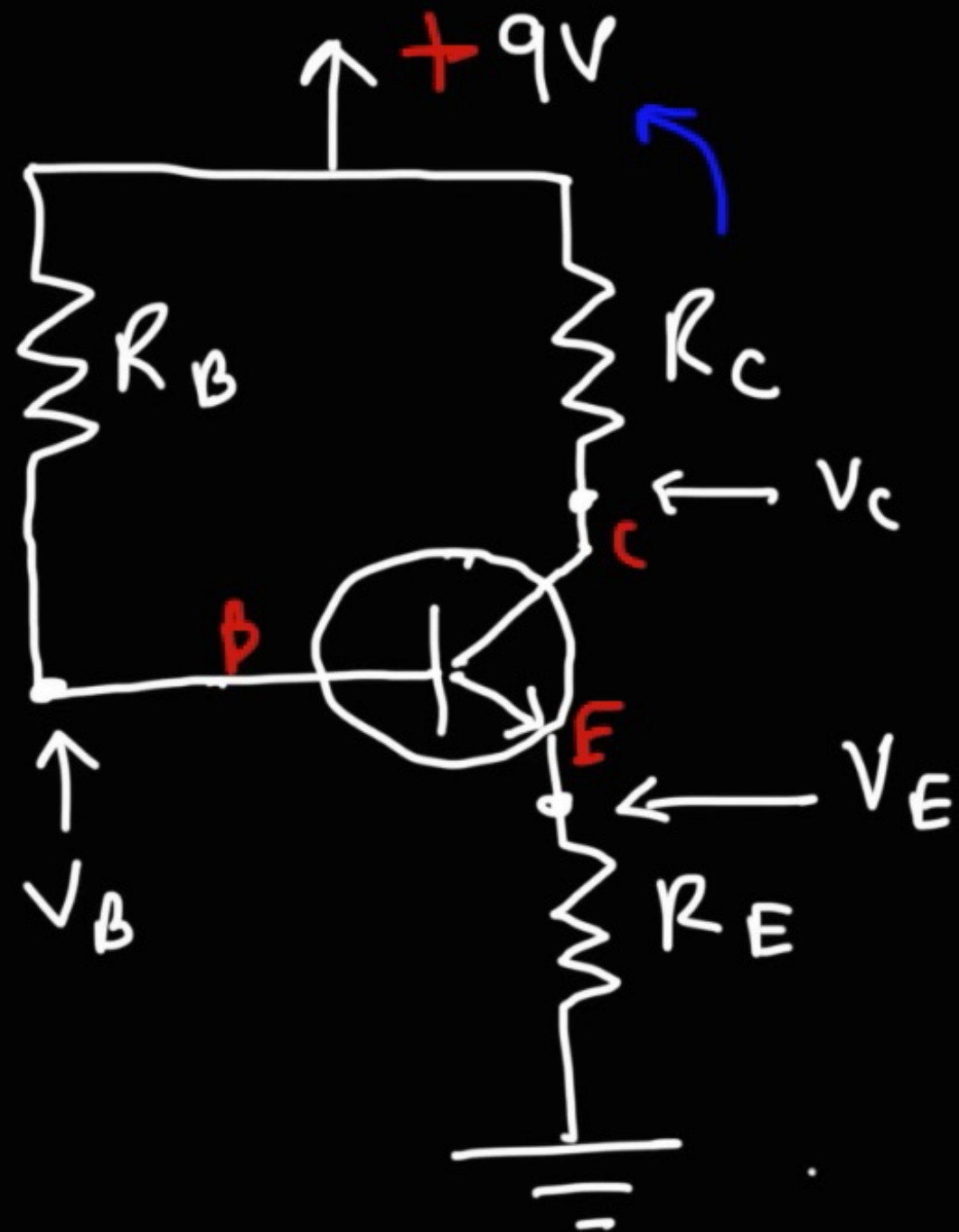

$$V_{CE} = V_C - V_E$$

$$V_{BE} = V_B - V_E =$$

$$0.6 - 0.7 \text{ V}$$


$$V_{CB} = V_C - V_B$$

$$V_{CC} = +9 \text{ V}$$

$$V_{EE} = 0 \text{ V}$$

V_{BE} harus bernilai tersebut agar ON

Transistor: Identification

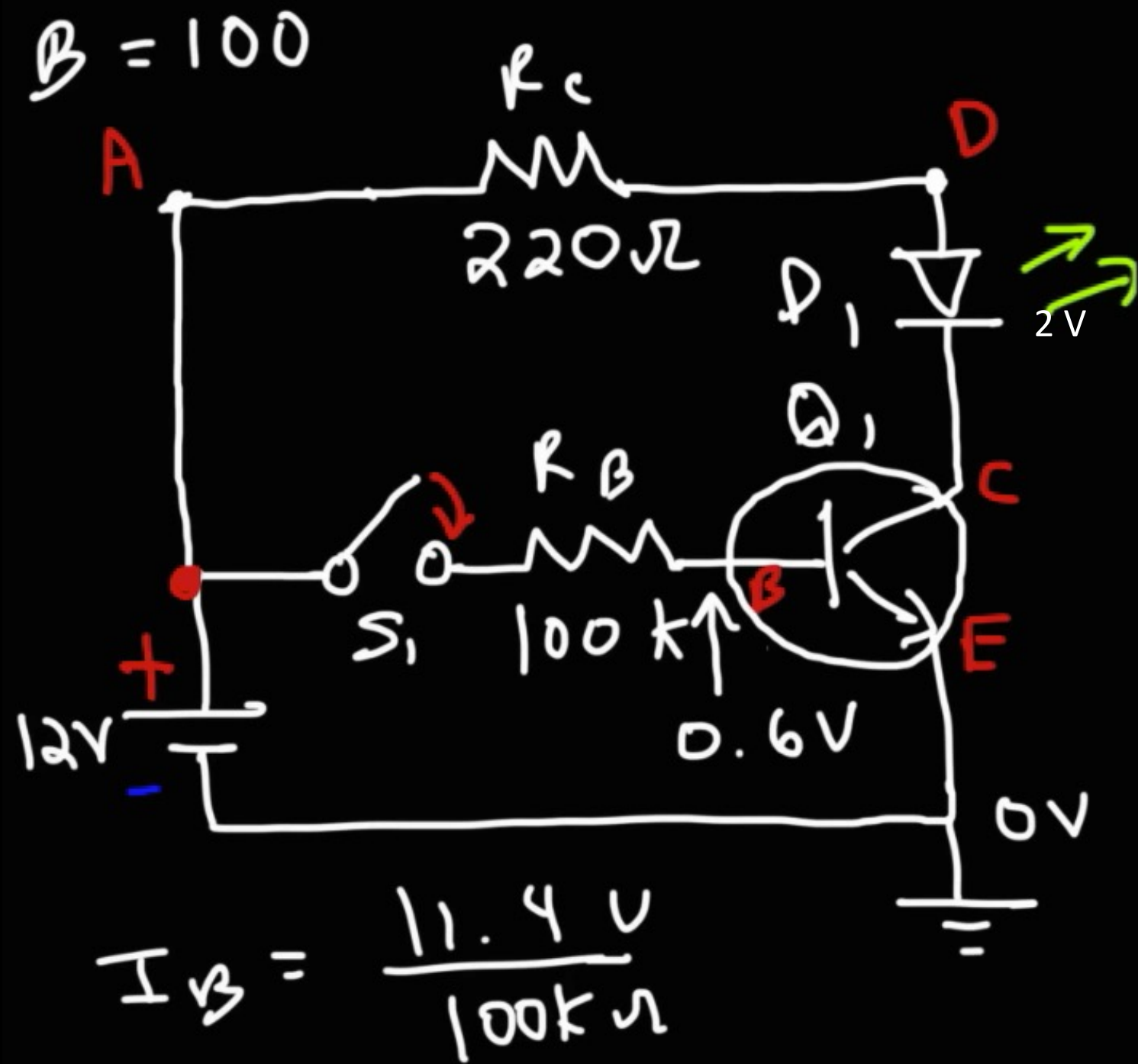

$V_{BE} = 0.6V$

$I_B = 0.114mA$

R_B


12V

0.6V

$I_B = \frac{12V - 0.6V}{100k}$

$I_B = \frac{V_A - V_B}{R_B}$


Transistor: Identification

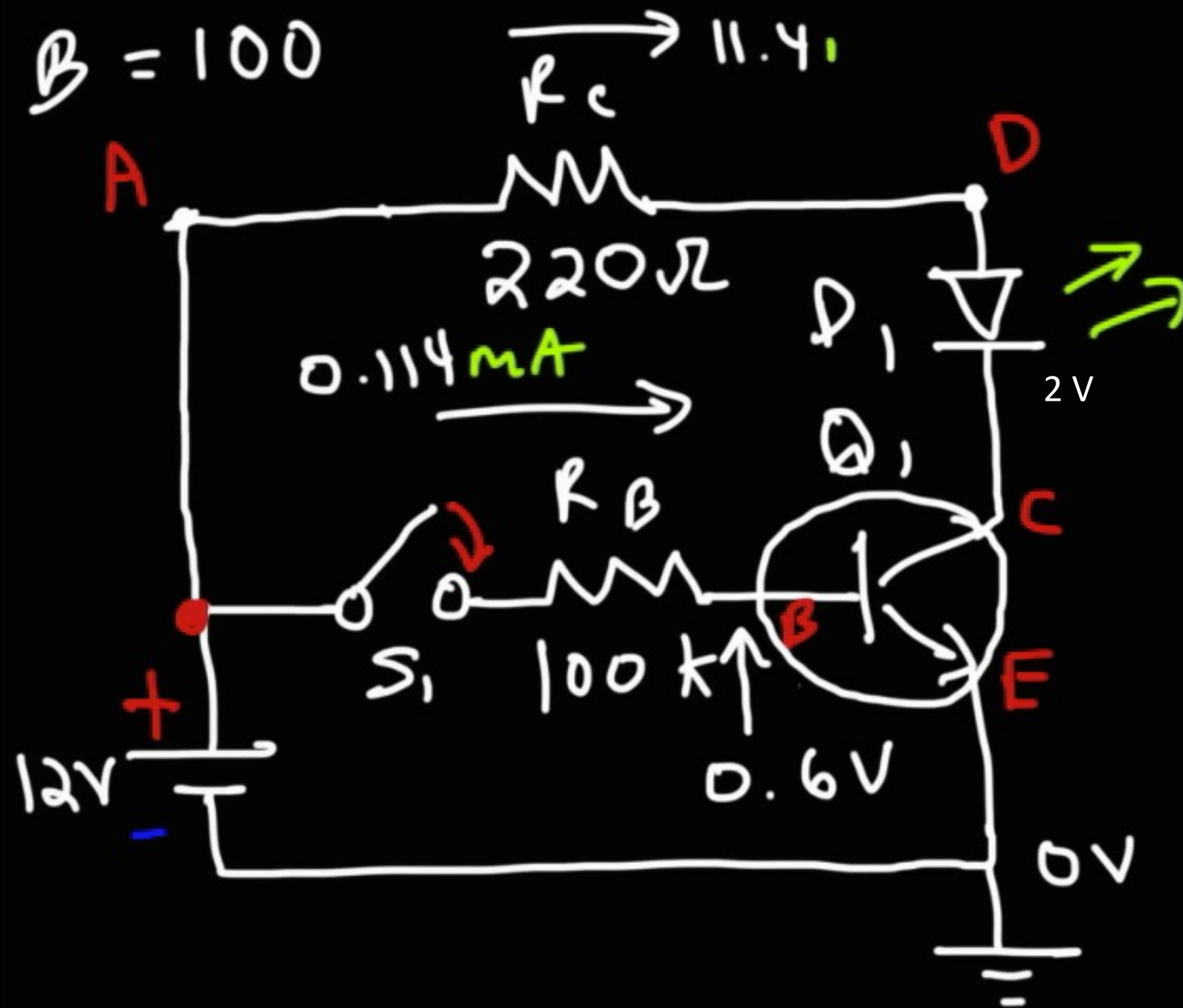

$$V_{BE} = 0.6V$$
$$I_B = 0.114mA$$


$$I_C = \beta I_B$$
$$= 100 (0.114mA)$$
$$I_C = 11.4mA$$

Transistor: Identification

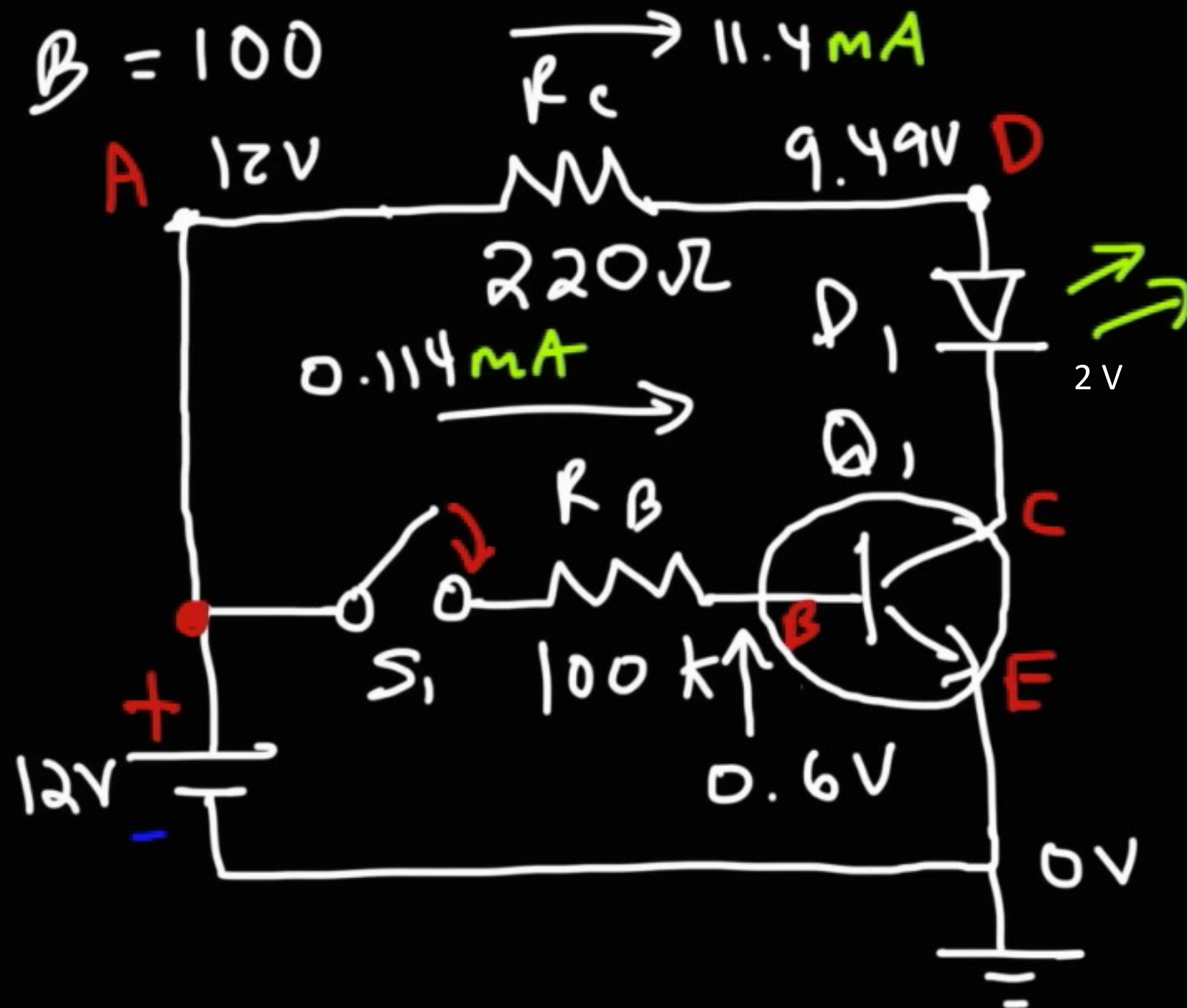

$$\Delta V = I R$$
$$V_A - V_D = I_c R_c$$
$$V_D = V_A - I_c R_c$$
$$V_D = 12 - (0.0114)(220)$$
$$V_D = 9.492V$$


Transistor: Identification

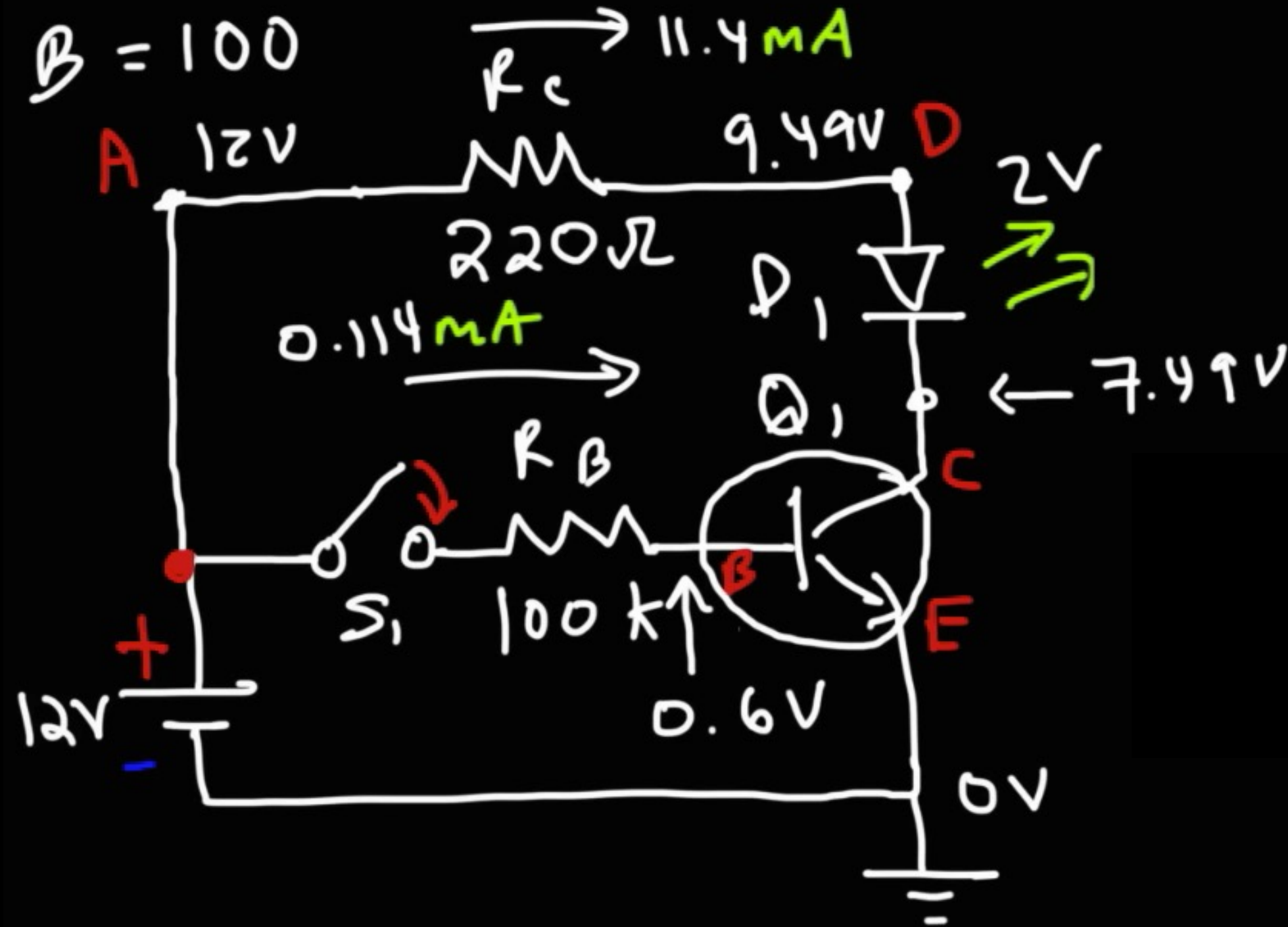

$$V_{CE} = 7.49 \text{ V}$$

Transistor: Region

CUTOFF

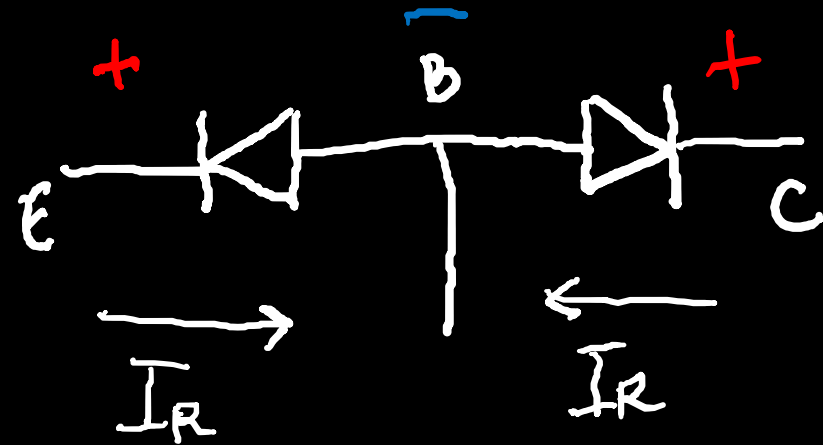

$$\Rightarrow V_B < V_E ; V_B < 0,6V$$

Maka, berlaku reverse biased pada E-B junction


$$\Rightarrow V_B < V_C ; V_{CE} = V_{CC}$$

Maka, berlaku reverse biased pada C-B junction

$$\Rightarrow I_C \approx 0A$$

Transistor OFF -> OPEN SWITCH

ACTIVE

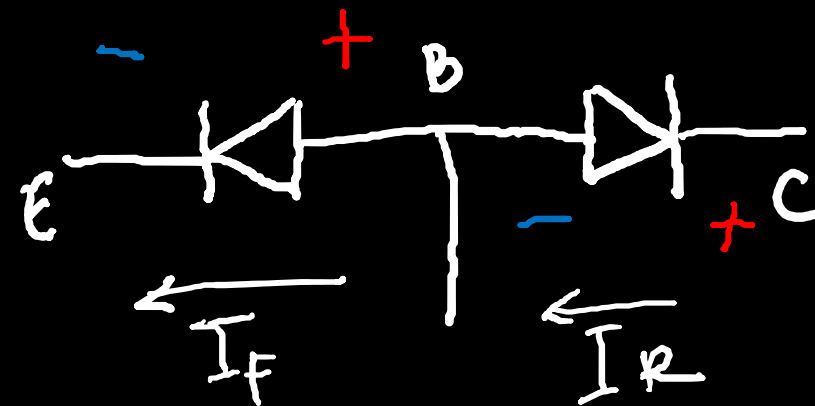

$$\Rightarrow V_{BE} \geq 0,6V$$

Maka, berlaku forward biased pada E-B junction


$$\Rightarrow V_B < V_C ; 0 < V_{CE} < V_{CC}$$

Maka, berlaku reverse biased pada C-B junction

$$\Rightarrow 0 < I_C < I_{sat} ; I_C = \beta \cdot I_B$$

Transistor = Amplifier

SATURATION

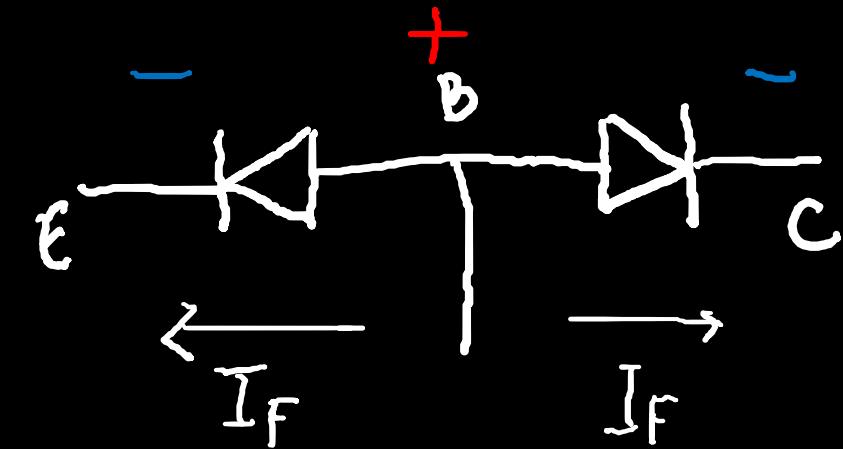

$$\Rightarrow V_{BE} \geq 0,6V$$

Maka, berlaku forward biased pada E-B junction


$$\Rightarrow V_{CE} \approx 0V$$

Maka, berlaku forward biased pada C-B junction

$$\Rightarrow I_C \approx I_{C(sat)}$$

$$\hookrightarrow I_{C(sat)} = \frac{\Delta V}{\Sigma R} = \frac{V_{CC} - V_D}{R_C}$$

Transistor ON -> CLOSED SWITCH

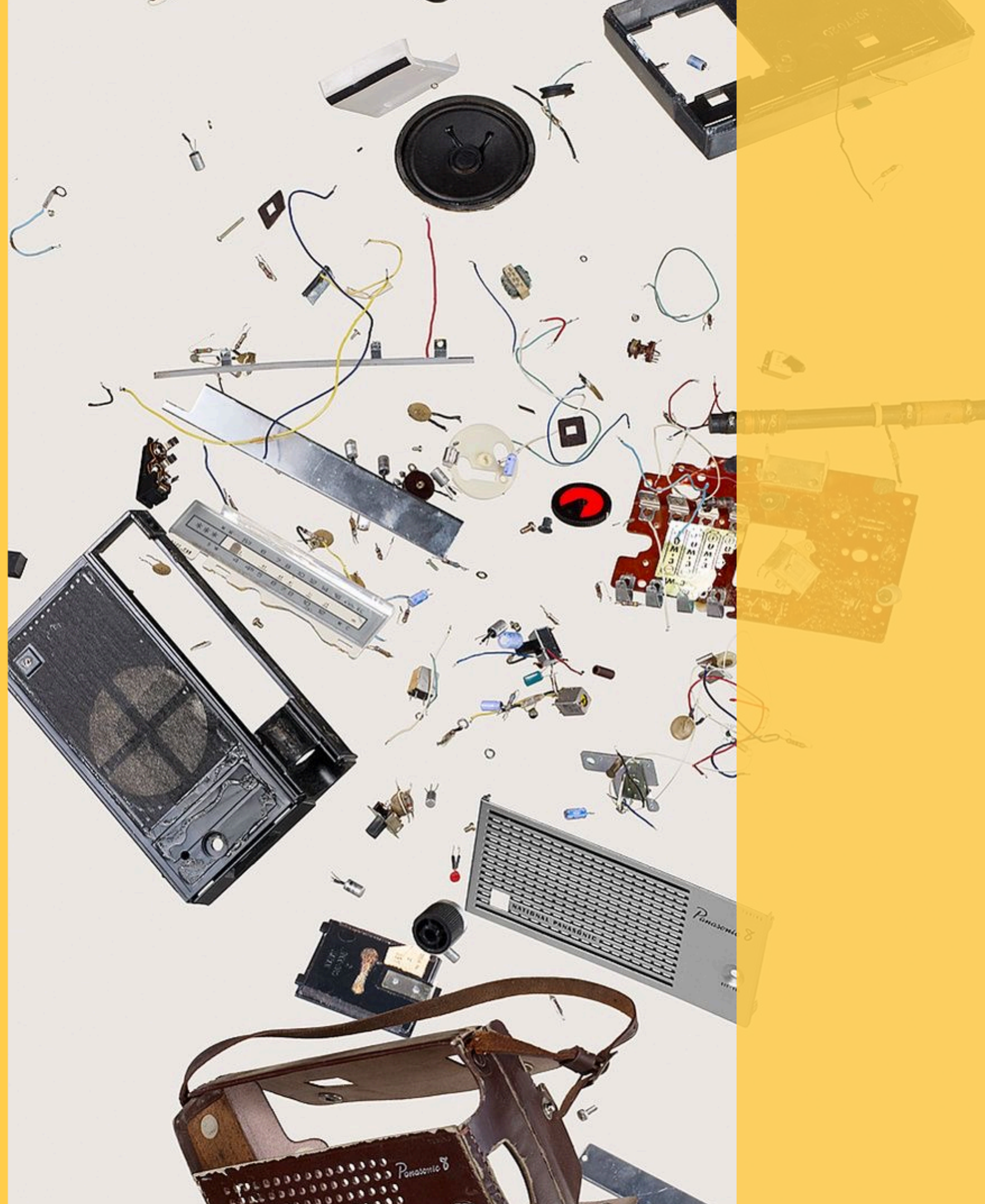

- END -