

Resonansi

Suatu rangkaian dikatakan beresonansi ketika tegangan terpasang V dan arus yang dihasilkan I dalam kondisi satu fasa.

Misalkan :

$$V = A \angle \alpha^\circ$$

$$I = B \angle \beta^\circ$$

Dalam kondisi satu fasa : $\alpha^\circ = \beta^\circ$, sehingga :

$$Z = \frac{V}{I} = \frac{A \angle \alpha^\circ}{B \angle \beta^\circ} = \frac{A}{B} \angle (\alpha^\circ - \beta^\circ) = \frac{A}{B} \angle 0^\circ = \frac{A}{B}$$

Terlihat bahwa ketika V dan I satu fasa, impedansi yang dihasilkan seluruhnya komponen riil atau impedansi kompleks hanya terdiri dari komponen resistor murni (R). Dengan kata lain konsep resonansi adalah menghilangkan komponen imajiner / reaktansi saling meniadakan.

Resonansi Seri

Impedansi total:

$$\mathbf{Z}_{tot} = R + j \left(\omega L - \frac{1}{\omega C} \right)$$


saat resonansi :

$$\omega L - \frac{1}{\omega C} = 0 \rightarrow \omega L = \frac{1}{\omega C}$$

$$\omega^2 = \frac{1}{LC}$$

$$f_o = \frac{1}{2\pi} \frac{1}{\sqrt{LC}}$$

Pada saat resonansi impedansi $\mathbf{Z}$ minimum, sehingga arusnya maksimum.

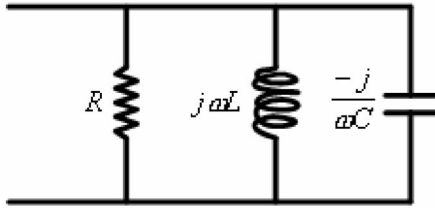Resonansi Paralel

Admitansi total :

$$\frac{1}{\mathbf{Z}_{tot}} = \frac{1}{R} + \frac{1}{j\omega L} + \frac{1}{-j/\omega C} = \frac{1}{R} - \frac{j}{\omega L} + j\omega C$$

$$\frac{1}{\mathbf{Z}_{tot}} = \frac{1}{R} + j\left(\omega C - \frac{1}{\omega L}\right)$$

saat resonansi :


$$\omega C - \frac{1}{\omega L} = 0 \rightarrow \omega C = \frac{1}{\omega L}$$

$$\omega^2 = \frac{1}{LC}$$

$$f_o = \frac{1}{2\pi} \frac{1}{\sqrt{LC}}$$

Pada saat resonansi impedansi $\mathbf{Z}$ maksimum, sehingga arusnya minimum.

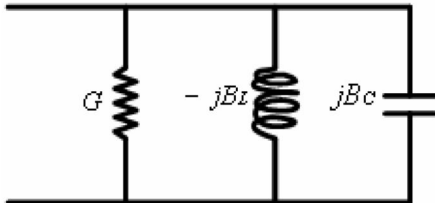Gambar tersebut dapat diganti notasinya :



Admitansi total :

$$Y = G + jB_C - jB_L$$

$$Y = G + j\left(\omega C - \frac{1}{\omega L}\right)$$


saat resonansi :

$$\omega C - \frac{1}{\omega L} = 0 \rightarrow \omega C = \frac{1}{\omega L}$$

$$\omega^2 = \frac{1}{LC}$$

$$f_o = \frac{1}{2\pi} \frac{1}{\sqrt{LC}}$$

Resonansi Paralel 2 Cabang

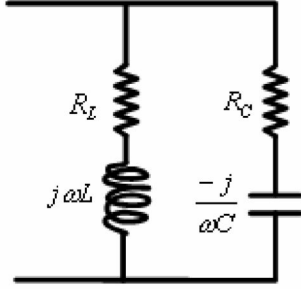

$$\frac{1}{\mathbf{Z}_{tot}} = \frac{1}{R_L + j\omega L} + \frac{1}{R_C - \frac{j}{\omega C}}$$

$$\frac{1}{\mathbf{Z}_{tot}} = \frac{1}{R_L + j\omega L} \left(\frac{R_L - j\omega L}{R_L - j\omega L} \right) + \frac{1}{R_C - \frac{j}{\omega C}} \left(\frac{R_C + \frac{j}{\omega C}}{R_C + \frac{j}{\omega C}} \right)$$

$$\frac{1}{\mathbf{Z}_{tot}} = \frac{R_L - j\omega L}{R_L^2 + (\omega L)^2} + \frac{R_C + \frac{j}{\omega C}}{R_C^2 + \left(\frac{1}{\omega C}\right)^2}$$

$$\frac{1}{\mathbf{Z}_{tot}} = \frac{R_L}{R_L^2 + (\omega L)^2} + \frac{R_C}{R_C^2 + \left(\frac{1}{\omega C}\right)^2} + j \left(\frac{\frac{1}{\omega C}}{R_C^2 + \left(\frac{1}{\omega C}\right)^2} - \frac{\omega L}{R_L^2 + (\omega L)^2} \right)$$

saat resonansi:

$$\frac{\frac{1}{\omega C}}{R_C^2 + \left(\frac{1}{\omega C}\right)^2} - \frac{\omega L}{R_L^2 + (\omega L)^2} = 0$$

$$\frac{\frac{1}{\omega C}}{R_C^2 + \left(\frac{1}{\omega C}\right)^2} = \frac{\omega L}{R_L^2 + (\omega L)^2}$$

$$R_L^2 + (\omega L)^2 = \omega^2 LC \left(R_C^2 + \left(\frac{1}{\omega C}\right)^2 \right)$$

$$R_L^2 + \omega^2 L^2 = \omega^2 LC R_C^2 + \frac{L}{C}$$

$$\omega^2 LC R_C^2 - \omega^2 L^2 = R_L^2 - \frac{L}{C}$$

$$\omega^2 LC \left(R_C^2 - \frac{L}{C} \right) = R_L^2 - \frac{L}{C}$$


$$f_o = \frac{1}{2\pi\sqrt{LC}} \sqrt{\frac{R_L^2 - \frac{L}{C}}{R_C^2 - \frac{L}{C}}}$$

Perlu diingat bahwa : $\sqrt{\frac{R_L^2 - \frac{L}{C}}{R_C^2 - \frac{L}{C}}}$ harus positif real sehingga syarat :

$$R_L^2 > \frac{L}{C} \text{ dan } R_C^2 > \frac{L}{C} \text{ atau } R_L^2 < \frac{L}{C} \text{ dan } R_C^2 < \frac{L}{C}$$

Ketika nilai $R_L^2 = R_C^2 = \frac{L}{C}$, maka rangkaian beresonansi untuk semua frekuensi.

Resonansi Kombinasi 1

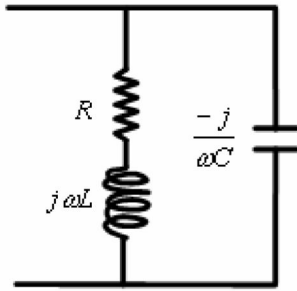

$$\mathbf{Z}_1 = R + j\omega L$$

$$\mathbf{Z}_2 = \frac{1}{j\omega C}$$

$$\frac{1}{\mathbf{Z}_{tot}} = \frac{1}{\mathbf{Z}_1} + \frac{1}{\mathbf{Z}_2} = \frac{1}{R + j\omega L} + \frac{1}{\frac{1}{j\omega C}} = \frac{1}{R + j\omega L} + j\omega C$$

$$\frac{1}{\mathbf{Z}_{tot}} = j\omega C + \frac{1}{R + j\omega L} \left(\frac{R - j\omega L}{R - j\omega L} \right)$$

$$\frac{1}{\mathbf{Z}_{tot}} = j\omega C + \frac{R - j\omega L}{R^2 + \omega^2 L^2}$$


$$\frac{1}{\mathbf{Z}_{tot}} = \frac{R}{R^2 + \omega^2 L^2} + j \left(\omega C - \frac{\omega L}{R^2 + \omega^2 L^2} \right)$$

saat resonansi : $\omega_C = \frac{\omega_L}{R^2 + \omega^2 L^2}$, sehingga :

$$R^2 + \omega^2 L^2 = \frac{L}{C} \rightarrow \omega^2 L^2 = \frac{L}{C} - R^2 \rightarrow \omega^2 = \frac{1}{L^2} \left(\frac{L}{C} - R^2 \right) = \frac{1}{LC} - \frac{R^2}{L^2} = \frac{1}{LC} \left(1 - \frac{R^2 C}{L} \right)$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}} \sqrt{\left(1 - \frac{R^2 C}{L} \right)}$$

Resonansi Kombinasi 2

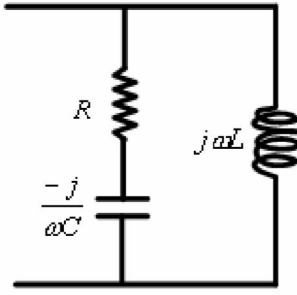

$$\mathbf{Z}_1 = R + \frac{1}{j\omega C} = R - \frac{j}{\omega C}$$

$$\mathbf{Z}_2 = j\omega L$$

$$\frac{1}{\mathbf{Z}_{tot}} = \frac{1}{\mathbf{Z}_1} + \frac{1}{\mathbf{Z}_2} = \frac{1}{R - \frac{j}{\omega C}} + \frac{1}{j\omega L} = \frac{1}{R - \frac{j}{\omega C}} - \frac{j}{\omega L}$$

$$\frac{1}{\mathbf{Z}_{tot}} = \frac{1}{R - \frac{j}{\omega C}} \left(\frac{R + \frac{j}{\omega C}}{R + \frac{j}{\omega C}} \right) - \frac{j}{\omega L} = \frac{R + \frac{j}{\omega C}}{R^2 + \frac{1}{\omega^2 C^2}} - \frac{j}{\omega L}$$

$$\frac{1}{\mathbf{Z}_{tot}} = \frac{R}{R^2 + \frac{1}{\omega^2 C^2}} + j \left(\frac{\frac{1}{\omega C}}{R^2 + \frac{1}{\omega^2 C^2}} - \frac{1}{\omega L} \right)$$


saat resonansi : $\frac{\frac{1}{\omega C}}{R^2 + \frac{1}{\omega^2 C^2}} = \frac{1}{\omega L}$, sehingga :

$$R^2 + \frac{1}{\omega^2 C^2} = \frac{L}{C} \rightarrow \frac{1}{\omega^2 C^2} = \frac{L}{C} - R^2 \rightarrow \omega^2 C^2 = \frac{1}{\frac{L}{C} - R^2} \rightarrow \omega^2 = \frac{1}{C^2 \left(\frac{L}{C} - R^2 \right)}$$

$$\omega^2 = \frac{1}{LC - C^2 R^2} = \frac{1}{LC \left(1 - \frac{CR^2}{L} \right)}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}} \sqrt{\frac{1}{\left(1 - \frac{CR^2}{L} \right)}}$$

Resonansi Kombinasi 3

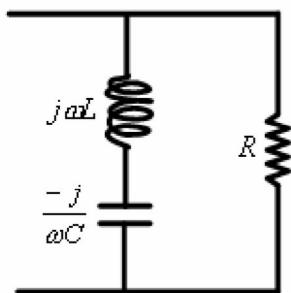

$$\mathbf{Z}_1 = j\omega L + \frac{1}{j\omega C}$$

$$\mathbf{Z}_2 = R$$


$$\frac{1}{\mathbf{Z}_{tot}} = \frac{1}{\mathbf{Z}_1} + \frac{1}{\mathbf{Z}_2} = \frac{1}{j\omega L + \frac{1}{j\omega C}} + \frac{1}{R} = \frac{1}{R} - \frac{j\omega C}{1 - \omega^2 LC}$$

saat resonansi :

$$\frac{\omega C}{1 - \omega^2 LC} = 0$$

$$f_0 = 0$$

Resonansi Kombinasi 4

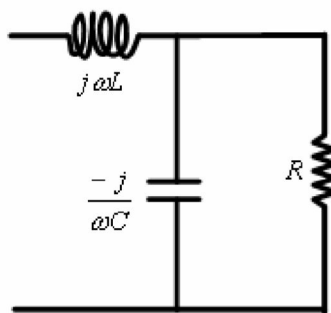

$$\frac{1}{\mathbf{Z}_1} = \frac{1}{R} + \frac{1}{\frac{1}{j\omega C}} = \frac{1}{R} + j\omega C \rightarrow \mathbf{Z}_1 = \frac{1}{\frac{1}{R} + j\omega C}$$

$$\mathbf{Z}_2 = j\omega L$$

$$\mathbf{Z}_{tot} = \mathbf{Z}_1 + \mathbf{Z}_2 = \frac{1}{\frac{1}{R} + j\omega C} + j\omega L$$

$$\mathbf{Z}_{tot} = j\omega L + \frac{1}{\frac{1}{R} + j\omega C} \left(\frac{\frac{1}{R} - j\omega C}{\frac{1}{R} - j\omega C} \right) = j\omega L + \frac{\frac{1}{R} - j\omega C}{\frac{1}{R^2} + \omega^2 C^2}$$

$$\mathbf{Z}_{tot} = \frac{\frac{1}{R}}{\frac{1}{R^2} + \omega^2 C^2} + j \left(\omega L - \frac{\omega C}{\frac{1}{R^2} + \omega^2 C^2} \right)$$


saat resonansi : $\omega L = \frac{\omega C}{\frac{1}{R^2} + \omega^2 C^2}$, sehingga :

$$\frac{1}{R^2} + \omega^2 C^2 = \frac{C}{L} \rightarrow \omega^2 C^2 = \frac{C}{L} - \frac{1}{R^2}$$

$$\omega^2 = \frac{1}{C^2} \left(\frac{C}{L} - \frac{1}{R^2} \right) = \frac{1}{LC} - \frac{1}{C^2 R^2} = \frac{1}{LC} \left(1 - \frac{L}{CR^2} \right)$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}} \sqrt{1 - \frac{L}{CR^2}}$$

Resonansi Kombinasi 5

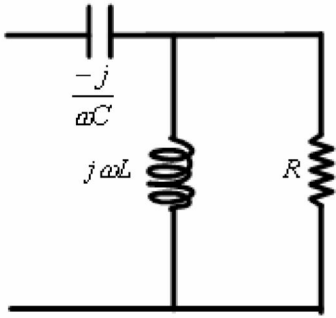

$$\frac{1}{\mathbf{Z}_1} = \frac{1}{R} + \frac{1}{j\omega L} = \frac{1}{R} - \frac{j}{\omega L} \rightarrow \mathbf{Z}_1 = \frac{1}{\frac{1}{R} - \frac{j}{\omega L}}$$

$$\mathbf{Z}_2 = \frac{1}{j\omega C} = -\frac{j}{\omega C}$$

$$\mathbf{Z}_{tot} = \mathbf{Z}_1 + \mathbf{Z}_2 = \frac{1}{\frac{1}{R} - \frac{j}{\omega L}} - \frac{j}{\omega C} = \frac{1}{\frac{1}{R} - \frac{j}{\omega L}} \left(\frac{\frac{1}{R} + \frac{j}{\omega L}}{\frac{1}{R} + \frac{j}{\omega L}} \right) - \frac{j}{\omega C}$$

$$\mathbf{Z}_{tot} = \frac{\frac{1}{R} + \frac{j}{\omega L}}{\frac{1}{R^2} + \frac{1}{\omega^2 L^2}} - \frac{j}{\omega C} = \frac{\frac{1}{R}}{\frac{1}{R^2} + \frac{1}{\omega^2 L^2}} + j \left(\frac{\frac{1}{\omega L}}{\frac{1}{R^2} + \frac{1}{\omega^2 L^2}} - \frac{1}{\omega C} \right)$$


saat resonansi : $\frac{\frac{1}{\omega L}}{\frac{1}{R^2} + \frac{1}{\omega^2 L^2}} = \frac{1}{\omega C}$, sehingga :

$$\frac{1}{R^2} + \frac{1}{\omega^2 L^2} = \frac{C}{L} \rightarrow \frac{1}{\omega^2 L^2} = \frac{C}{L} - \frac{1}{R^2} \rightarrow \omega^2 L^2 = \frac{1}{\frac{C}{L} - \frac{1}{R^2}}$$

$$\omega^2 = \frac{1}{L^2 \left(\frac{C}{L} - \frac{1}{R^2} \right)} = \frac{1}{LC \left(1 - \frac{L}{CR^2} \right)}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}} \sqrt{\frac{1}{1 - \frac{L}{CR^2}}}$$

Resonansi Kombinasi 6

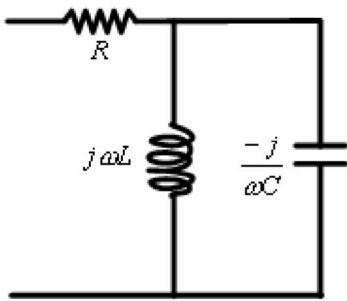

$$\frac{1}{\mathbf{Z}_1} = \frac{1}{j\omega L} + \frac{1}{\frac{1}{j\omega C}} = \frac{1}{j\omega L} + j\omega C \rightarrow \mathbf{Z}_1 = \frac{1}{\frac{1}{j\omega L} + j\omega C}$$

$$\mathbf{Z}_2 = R$$


$$\mathbf{Z}_{tot} = \mathbf{Z}_1 + \mathbf{Z}_2 = \frac{1}{\frac{1}{j\omega L} + j\omega C} + R = R + \frac{j\omega L}{1 - \omega^2 LC}$$

saat resonansi :

$$\frac{\omega L}{1 - \omega^2 LC} = 0$$

$$f_0 = 0$$

Resonansi Paralel 3 Cabang

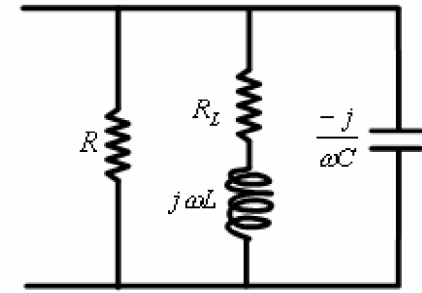

$$\mathbf{Z}_1 = R_L + j\omega L$$

$$\mathbf{Z}_2 = R$$

$$\mathbf{Z}_3 = \frac{1}{j\omega C}$$

$$\frac{1}{\mathbf{Z}_{tot}} = \frac{1}{\mathbf{Z}_1} + \frac{1}{\mathbf{Z}_2} + \frac{1}{\mathbf{Z}_3} = \frac{1}{R_L + j\omega L} + \frac{1}{R} + \frac{1}{\frac{1}{j\omega C}}$$

$$\frac{1}{\mathbf{Z}_{tot}} = \frac{1}{R} + j\omega C + \frac{1}{R_L + j\omega L} = \frac{1}{R} + j\omega C + \frac{1}{R_L + j\omega L} \left(\frac{R_L - j\omega L}{R_L - j\omega L} \right)$$

$$\frac{1}{\mathbf{Z}_{tot}} = \frac{1}{R} + j\omega C + \frac{R_L - j\omega L}{R_L^2 + \omega^2 L^2} = \frac{1}{R} + \frac{R_L}{R_L^2 + \omega^2 L^2} + j \left(\omega C - \frac{\omega L}{R_L^2 + \omega^2 L^2} \right)$$

saat resonansi : $\omega C = \frac{\omega L}{R_L^2 - \omega^2 L^2}$, sehingga :

$$R_L^2 + \omega^2 L^2 = \frac{L}{C} \rightarrow \omega^2 L^2 = \frac{L}{C} - R_L^2$$

$$\omega^2 = \frac{1}{L^2} \left(\frac{L}{C} - R_L^2 \right) = \frac{1}{LC} - \frac{R_L^2}{L^2} = \frac{1}{LC} \left(1 - \frac{CR_L^2}{L} \right)$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}} \sqrt{1 - \frac{CR_L^2}{L}}$$

Contoh latihan :

1. Suatu rangkaian seri RLC dengan $R = 50\Omega$, $L = 0,05H$, $C = 20\mu F$ terpasang pada $V = 100\angle 0^\circ$ dengan frekuensi variabel. Pada frekuensi berapa tegangan induktor mencapai maksimum ? Berapakah tegangan induktor tersebut ?
2. Tentukan frekuensi resonansi pada gambat berikut :

