



Teknik Digital

W6 - Reza Diharja, S.Si., M.T.

Outlines

6.1 Sum of Product

6.1.1 Minterm

6.1.2 Canonical SOP Form

6.1.3 Non-Canonical SOP Form

6.1.4 Schematic Design of Sum Of Product (SOP)

6.2 Product of Sum

6.2.1 Maxterm

6.2.2 Canonical POS

6.2.3 Non-Canonical Form

6.2.4 Minimal POS Form

6.2.5 Schematic Design of Product of Sum (POS)

Simplification Techniques

- Terdapat suatu cara yang bukan merupakan aplikasi dari hukum-hukum dan teorema bilangan Boolean.
- **Tujuan dari proses simplifikasi atau penyederhanaan adalah untuk menghasilkan suatu ekspresi yang memiliki sedikit bentuk istilah bilangan.** Mendapatkan ekspresi dengan jumlah literal yang sedikit merupakan tujuan lainnya.
- *If there is more than one possible solution with the same number of terms, the one having the minimum number of literals is the choice.*
- Teknik-teknik tersebut adalah **Quine-McCluskey metode tabel** dan **metode peta Karnaugh**.
- Namun sebelum menjalankannya, harus terlebih dahulu mengetahui ekspresi Boolean dalam bentuk **Sum of Product (SoP)** dan **Product of Sum (PoS)**.

Sum of Product (SOP)

- **Sum of Product** is the abbreviated form of **SOP**. Sum of product form is a form of expression in Boolean algebra in **which different product terms of inputs are being summed together**. This product is not arithmetical multiply but **it is Boolean logical AND and the Sum is Boolean logical OR**.
- There are few different forms of Sum of Product:
 - **Canonical** SOP Form
 - **Non-Canonical** SOP Form
 - **Minimal** SOP Form
- To understand better about SOP, we need to know about **min term**.

Minterm

- **Minterm means the term that is true for a minimum number of combination of inputs. That is true for only one combination of inputs.**
- Since **AND gate** also gives True only when all of its inputs are true so we can say minterms are AND of input combinations like in the table given.
- 3 inputs have 8 different combinations. **Each combination has a minterms denoted by small m and its decimal combination number written in subscript.**
- Each of these minterms will be only true for the specific input combination.

$$Y = \bar{A} \cdot \bar{B} \cdot \bar{C} + \bar{A} \cdot B \cdot C + A \cdot B \cdot \bar{C} + A \cdot \bar{B} \cdot C$$

A	B	C	Y	Min term
0	0	0	1	$m_0 = \bar{A} \bar{B} \bar{C}$
0	0	1	0	$m_1 = \bar{A} \bar{B} C$
0	1	0	0	$m_2 = \bar{A} B \bar{C}$
0	1	1	1	$m_3 = \bar{A} B C$
1	0	0	0	$m_4 = A \bar{B} \bar{C}$
1	0	1	1	$m_5 = A \bar{B} C$
1	1	0	1	$m_6 = A B \bar{C}$
1	1	1	0	$m_7 = A B C$

Diambil yang ber-angka 1

Canonical SOP Form

- Merupakan model standar dari Sum of Product.
- *This is also known as Sum of Min terms or Canonical disjunctive normal form (CDNF).*
- *The “canonical” means “standardized” and “disjunctive” means “Logical OR union”.*
- *Canonical SOP expression is represented by summation sign Σ and minterms in the braces for which the output is true.*

For this function the canonical SOP expression is:

$$F = \sum(m_1, m_2, m_3, m_5)$$

Which means that the function is true for the min terms **{1, 2, 3, 5}**.

By expanding the summation we get:

$$F = m_1 + m_2 + m_3 + m_5$$

Now putting min terms in the expression:

$$F = \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}C$$

Canonical form contains all inputs either complemented or non-complemented in its product terms.

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

Non-Canonical SOP Form

- As the name suggests, this form is the non-standardized form of SOP expressions.
- The product terms are not the min terms but they are simplified.

Let's take the previous function in canonical form as an example.

$$F = \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}C$$

$$F = \bar{A}\bar{B}C + \bar{A}B(\bar{C} + C) + A\bar{B}C$$

$$F = \bar{A}\bar{B}C + \bar{A}B(1) + A\bar{B}C$$

$$F = \bar{A}\bar{B}C + \bar{A}B + A\bar{B}C$$

Coba perhatikan
beda-nya di bagian
mana?

The last expression is still in **Sum of Product form** but it obtained by **non-canonical or non-standardized form**.

Minimal SOP Form

- *This form is the most simplified SOP expression of a function. It is also a form of non-canonical form.*
- *Minimal SOP form can be made using Boolean algebraic theorems but it is very easily made using Karnaugh map (K-map).*
- *Minimal SOP form is preferred because it uses the minimum number of gates and input lines. Commercially beneficial because of its compact size, fast speed, and low fabrication cost.*
- *Let's take an example of the function given above in canonical form (next slide).*

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

		BC			
		00	01	11	10
A	0	0	1	1	1
	1	0	1	0	0



According to the K-map, the output expression will be:

$$F = \bar{B}C + \bar{A}B$$

This expression requires only two 2-input AND gates & one 2-input OR gate. However, the canonical form needs four 3-input AND gates & one 4-input OR gate, which is relatively more costly than minimal form implementation.

Schematic Design of Sum Of Product (SOP)

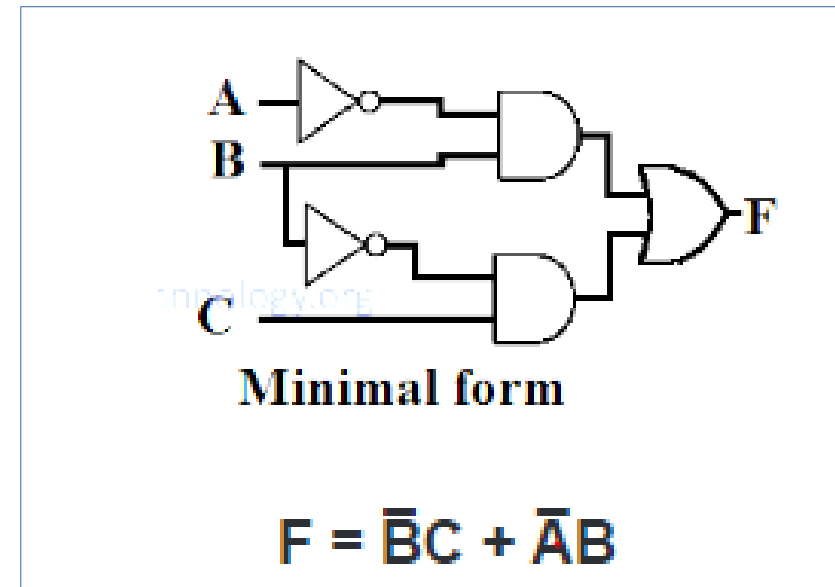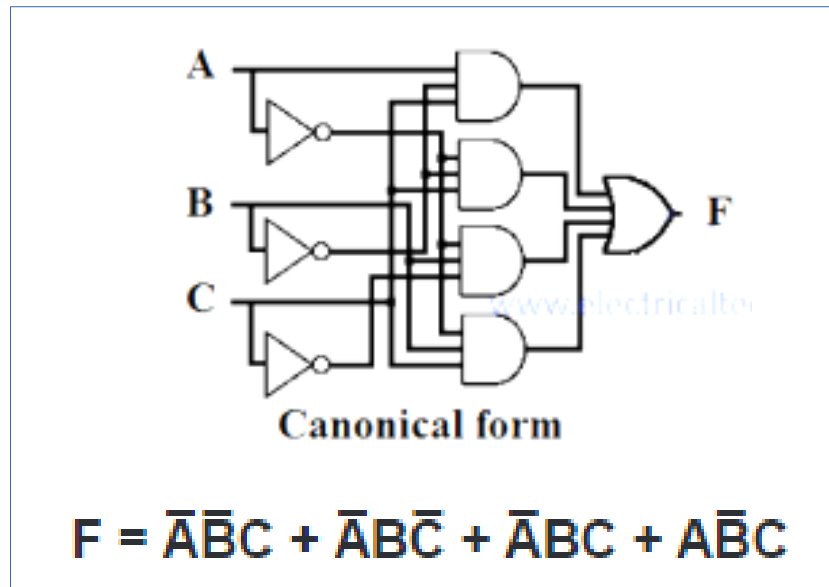- Example of designs of **canonical and minimal SOP** expression for a function is given below.



Mana yang lebih sederhana?
Apa alasannya?

Product of Sum (POS)

- *The product of Sum form is a form in which **products of different sum terms of inputs** are taken.*
- *These are not arithmetic product and sum but they are logical Boolean AND and OR respectively.*
- *To better understand about Product of Sum, we need to know about **maxterm**.*
- *Three types of POS:*
 - *Canonical POS Form*
 - *Non – Canonical Form*
 - *Minimal POS Form*

Maxterm

- *Maxterm means the **term or expression that is true for a maximum number of input combinations** or that is false for only one combination of inputs.*
- *Since OR gate also gives false for only one input combination. **Maxterm is OR of either complemented or non-complemented inputs.***
- *Max terms for 3 input variables are given side.*

A	B	C	Max term
0	0	0	$M_0 = A + B + C$
0	0	1	$M_1 = A + B + \bar{C}$
0	1	0	$M_2 = A + \bar{B} + C$
0	1	1	$M_3 = A + \bar{B} + \bar{C}$
1	0	0	$M_4 = \bar{A} + B + C$
1	0	1	$M_5 = \bar{A} + B + \bar{C}$
1	1	0	$M_6 = \bar{A} + \bar{B} + C$
1	1	1	$M_7 = \bar{A} + \bar{B} + \bar{C}$

Diambil yang ber-angka 0

- *In maxterm, each input is complemented because Maxterm gives '0' only when the mentioned combination is applied and **Maxterm is complement of minterm.***

$$M_3 = \bar{m}_3$$

$$M_3 = (\bar{A}BC)'$$

$$M_3 = A + \bar{B} + \bar{C} \quad \text{DE Morgan's law}$$

- Which is why for $A = 0$ Maxterm consist A & for $A = 1$ Maxterm consist .

Canonical POS

- It is also known as Product of Max term or Canonical conjunctive normal form (CCNF). Canonical means standard and conjunctive means intersection.
- In this form, **Maxterms are AND together for which output is false.**
- Canonical POS expression is represented by $\prod (p_i)$ and Maxterms for which output is false in brackets as shown in the example given table (next slide).

$$F = \prod (M_0, M_4, M_6, M_7)$$

Expanding the product

$$F = M_0 \cdot M_4 \cdot M_6 \cdot M_7$$

Putting Max terms:

$$F = (A+B+C)(\bar{A}+B+C)(\bar{A}+\bar{B}+C)(\bar{A}+\bar{B}+\bar{C})$$

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

Non-Canonical Form

- The product of sum expression that is not in standard form is called non-canonical form.
- Let's take the previous-given function as an example:

$$F = \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}C$$

Same but inverted terms eliminates from two Max terms and form a single term to prove it here is an example:

Minimal POS Form

- *This is the most simplified and optimized form of a POS expression which is non-canonical.*
- *Minimal Product of Sum form can be achieved using Boolean algebraic theorems like in the non-canonical example given before.*
- *Another method of achieving minimal POS form is by using Karnaugh map which is comparatively easier than using Boolean algebraic theorems.*
- *Minimal POS form uses less number of inputs and logic gates during its implementation, that's why they are being preferred over canonical form for their compact, fast and low-cost implementation.*

K-map of the function

Diambil yang ber-angka 0


		BC			
		00	01	11	10
A	0	0	1	1	1
	1	0	1	0	0

Minimal expression using K-map


$$F = (B+C) (\bar{A}+\bar{B})$$

- *The achieved expression is the minimal product of sum form.*
- *It is still Product of Sum expression But it needs only 2 inputs two OR gates and a single 2 input AND gate.*
- *However, the canonical form needs 4 OR gates of 3 inputs and 1 AND gate of 4 inputs.*

Schematic Design of Product of Sum (POS)

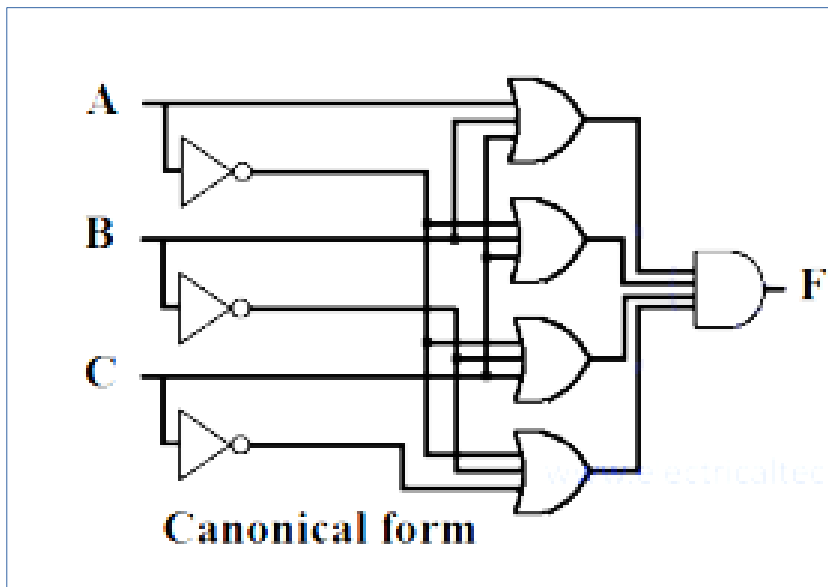
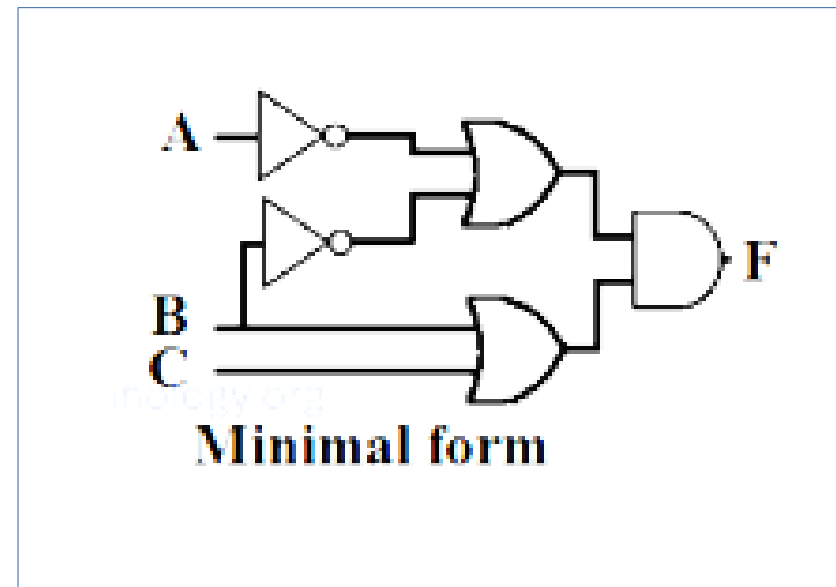
$$F = (A+B+C)(\bar{A}+B+C)(\bar{A}+\bar{B}+C)(\bar{A}+\bar{B}+\bar{C})$$



$$F = (B+C)(\bar{A}+\bar{B})$$

Mana yang lebih sederhana?
Apa alasannya?

Remaining Meeting Time: 01:44



Rezza Miftah Farizd



Reza Diharja



Marcos Pandapotan Siregar



Yopan Putra



TE Fiandra Rafly



TE RIVAL




TE HERMAN



Ahmad Frederick



Willy Situmorang

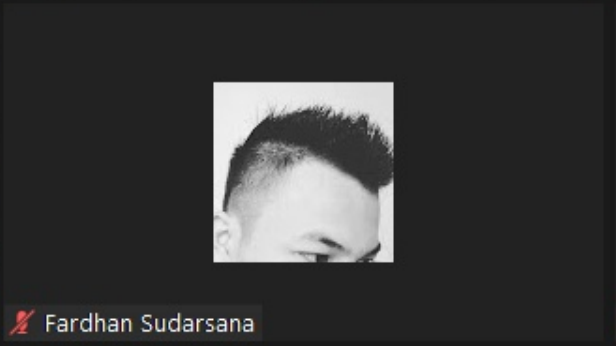

Fardhan Sudarsana



TE Ahmad Alfisyahr